

ECE 115C Final Project Report
Team #14: Lana Lim, Maria Campo Martins, Jared Velasquez

Phase	1	2	3
Analytical D(critical path)	39.79	N/A	55.71
Simulation D(critical path)	N/A	312.300615	559.40115
Analytical Energy	41.31	N/A	9.55
Simulation Energy	N/A	-0.99336	-0.2277408

Total Energy Reduction [%]	Contribution from sizing	Contribution from Vdd
Analytical model [%]	47.44	29.44
Simulation model [%]	19.79342836	57.28026094
Total delay increase [%]	Contribution from sizing	Contribution from Vdd
Analytical model [%]	18.4	21.6
Simulation model [%]	-8.124999049	48.124999049

Tables 1 and 2. Summary metrics.

 


Figure 1. Top-level diagram with highlighted critical path.


Gate	XOR0	XOR3	INV	CMP0	CMP1	CMP2	CMP3	CMP Cout
PMOS		778.09120 35	1009.0472 9	2617.0682 13	3394.0904 88	4401.4059 81	5708.1167 25	7402.4415 82
		224.95903 93	144.84940 27	237.63250 98	262.92365 65	374.34747 52	702.07767 06	1910.3683 58
	600							

NMOS		518.72746 9	672.69819 33	1744.7121 42	2262.7269 92	2934.2706 54	3805.4111 5	4934.9610 54
	400	149.97269 29	96.566268 48	158.42167 3	175.28243 77	249.56498 34	468.05178 04	1273.5789 06
TGATE		518.72746 9						
	400	149.97269 29						



Table 3. Baseline sizing in red. Optimal sizing in blue.

Critical path practical worst case delay:


 
- **x=1011, t=0010 with transitions at x0: 0->1 and t2: 1->0. Switching t2 does not affect critical path but allows us to measure the output transition more clearly.**
- **Test starts at 35ns.**
 - Baseline: 374.99785ps - 62.697235ps = **312.300615ps**



  - (Optimal) Sizing + VDD: 659.6984ps - 100.29725ps = **559.40115ps**



  - Sizing only: 344.09425ps - 57.168057ps = **286.926193ps**



Design decisions and rationale:

- Initially, we minimized the number of transistors by choosing optimal logic gates. E.g., transmission gate instead of CMOS XOR, comparators instead of full adders.
- Then we used truth tables to minimize the logic. E.g. adding 0001 does not actually require full adders. Since the input is fixed, we can simplify the logic down to 1 AND and 1 XOR gate for the non-fixed inputs.
- Finally, we identified points in the critical path where we could save time. E.g., by switching the order of inputs in an XOR gate, we could have the critical path going through a shorter stage.

Trade-offs to achieve design goals:

- Size vs. VDD: increasing sizing and decreasing width to make our energy consumption a lot lower but consequently increases our delay.
- Optimizing for the critical path vs. optimizing for the rest of the circuit: we didn't want to increase the delay of the other paths by so much that they would in turn become the critical path.